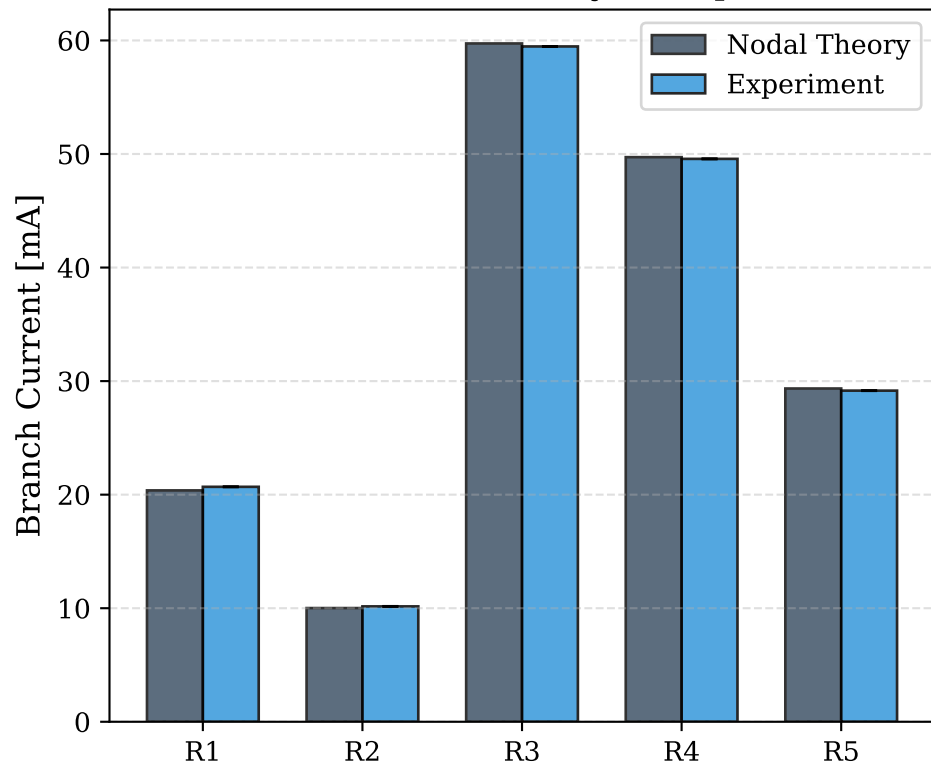


Branch Currents: Theory vs Experiment



Resistor Voltages: Theory vs Experiment

